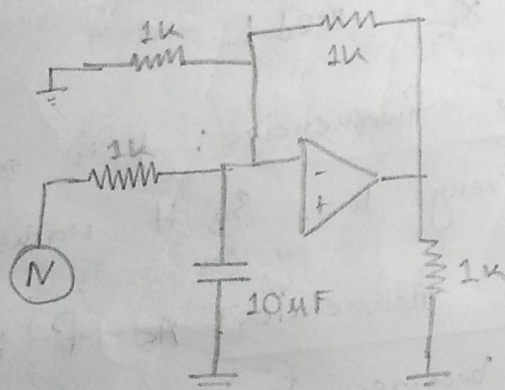


EEE-321


2102024- Md. Sharafat Karim

⊛ Is it possible to make low pass filter using inductor?


Ans: In general we can make a low pass filter with following configuration:



The output will be like,

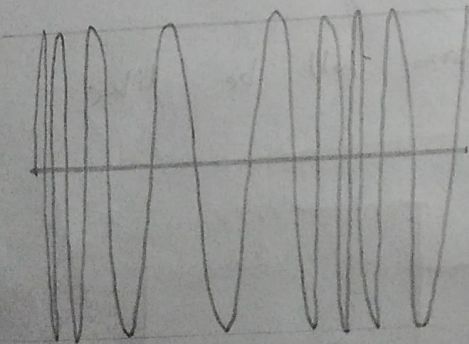

Input

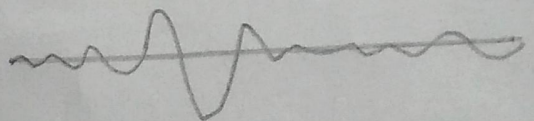

Output

Here, $A_v = \frac{V_o}{E_i} = \frac{1}{1 + j\omega RC}$

So, when $\omega \approx 0$, then $\frac{V_o}{E_i}$ is nearly 1


At high frequency ($\omega \rightarrow \infty$), and the $\frac{V_o}{E_i}$ becomes 0.


So, now if we want to use inductor instead of a conductor, we may need to put it in series with the input. Because the resistance of an inductor (X_L) is directly proportional to the frequency.

$$X_L = 2\pi f L$$


- ① At low frequencies: f is small, so X_L is very low. So it works like short circuit.
- ② At high frequencies: As f increases, X_L becomes large, which works like open circuit.

So our diagram will be like

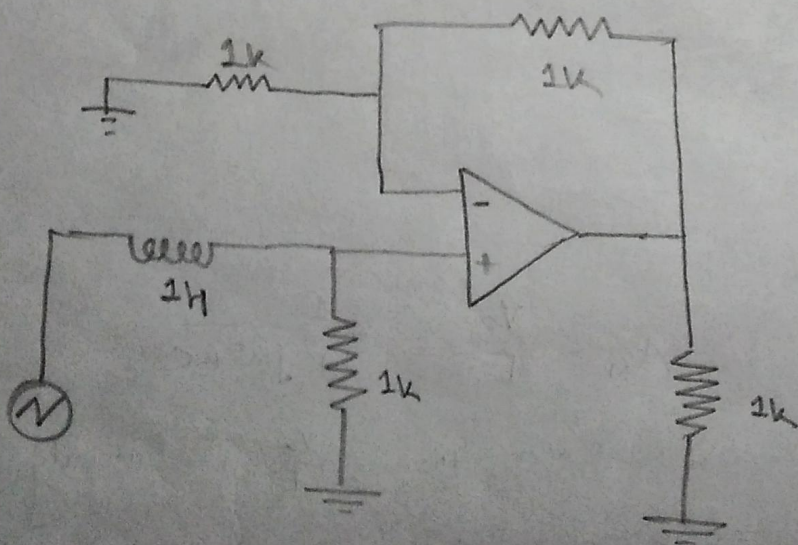

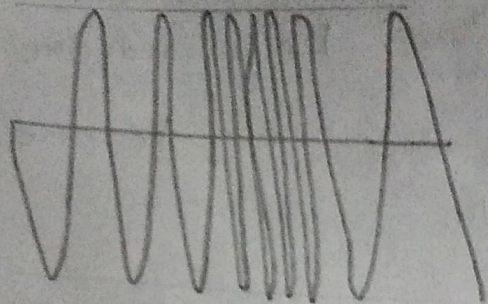

Input

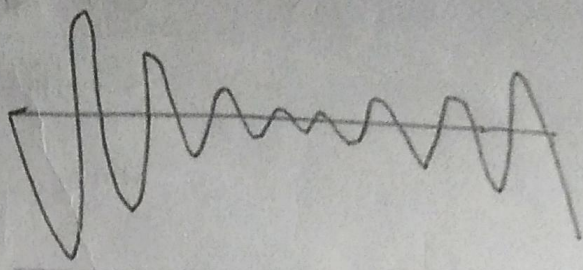

Output

The transfer function $\frac{V_{out}}{V_{in}} = \frac{R}{R + j\omega L}$

and the magnitude $\left| \frac{V_{out}}{V_{in}} \right| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$

At low frequency, $f=0$, $\omega=0$

$$\text{So, } \left| \frac{V_{out}}{V_{in}} \right| = \frac{R}{\sqrt{R^2 + 0}} = 1$$

So it will pass.

At high frequency, $f=\infty$ or $\omega=\infty$

$$\text{So, } \left| \frac{V_{out}}{V_{in}} \right| = \frac{R}{\sqrt{(\omega L)^2}} = 0$$

So it will be blocked.

□ So it is possible to make low pass filter with inductor. But it not practical. Here's some reasons:



① Internal resistance: Every inductor has significant resistance because of wire length.

② Size and cost: Inductors for low frequencies (like 100 mH or 1H) are physically huge, heavy and expensive.


③ Magnetic interference: Inductors are prone to electromagnetic interference (EMI). And they are also hard to implement in a silicon chip.

① Bandpass filter implementation.

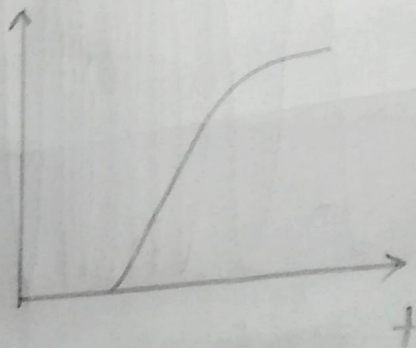
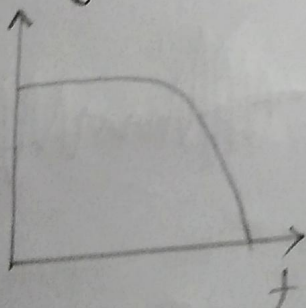
Ans: A low pass filter passes frequencies that are below the cutoff frequency, and a high pass filter passes frequencies that are above the cutoff frequency.



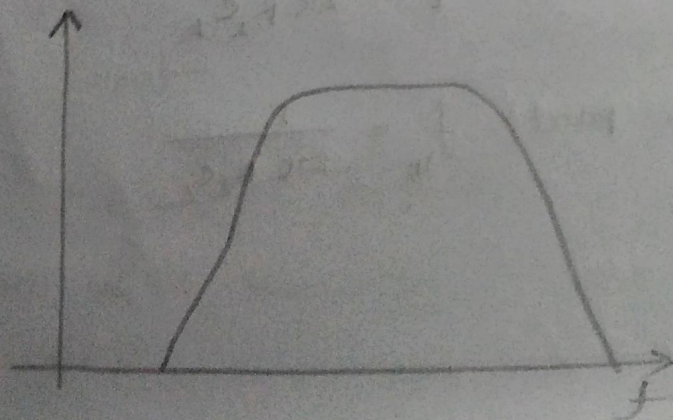
And in the band pass, it passes frequencies that fall only within a relatively narrow range.



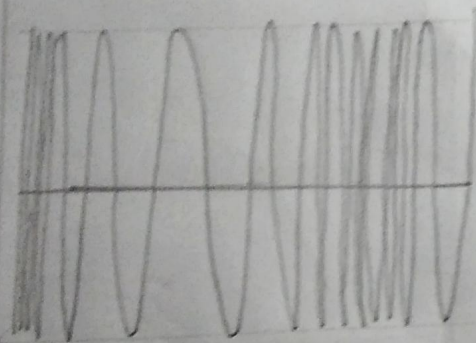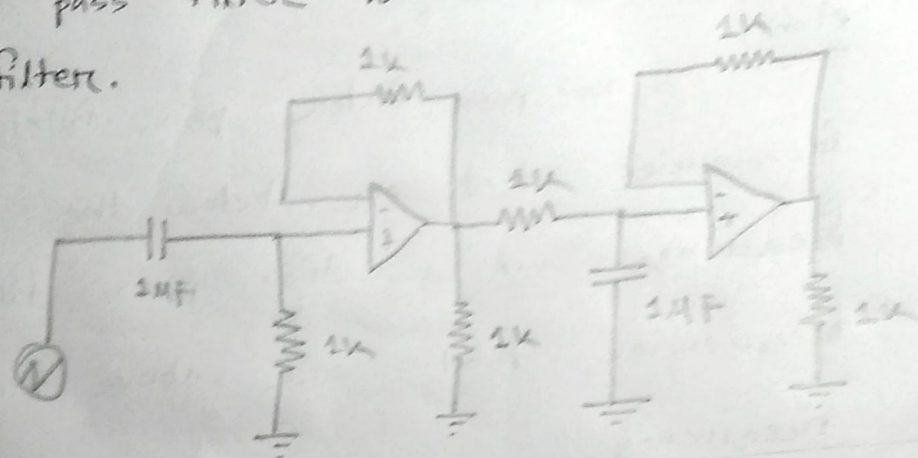So, we can combine both high pass filter and low pass filter to make a band-pass filter.



Input

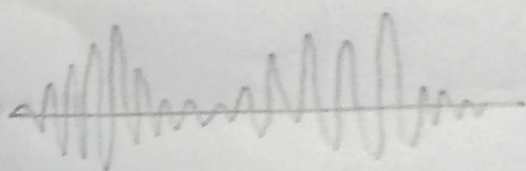

Output

So, the cutoff region, for

lower part
$$f_L = \frac{1}{2\pi R_1 C_1}$$

upper part
$$f_H = \frac{1}{2\pi R_2 C_2}$$